

Aayush Shah

19BCE245

22 September 2020

# Practical 5


## Practical 5 A&B

Design and Implementation of BCD and excess 3 parallel adder using two binary adders .


## OUTLINE :

- Snapshots of logisim
- Introduction and Conclusion [Design and implementation]
- Truth-Tables

## BINARY SUM TO BCD SUM

 

## EXCESS-3 PARALLEL ADDER

 

## Introduction 5A

The key purpose of this practice was the insertion of two binary numbers and give the output of their BCD sum. The numbers are from range 1 to 9 [binary : 0000 to 1001].

The BCD sum will be same as binary sum if the sum is less than or equal to 9 otherwise it will differ by 6.

## Conclusion 5A

From this practical , We learnt the usage of splitter and 4 bit adder. This experience gave us an insight into how to think critically according to our criteria for setting up a circuit. We learned to work out the conditions that would fulfil our output according to the inputs, we set up 3 conditions, which even one of them was valid than we would add 6 to the output of initial sums of input. This way, we conducted our practical 5(A) of obtaining BCD sum from binary sum along with their Design and Implementation.

## Introduction 5B

The main aim of this practical to add two 4 bit excess-3 parallel adder using two binary adders. The numbers can be from 0 to 9 [Binary : 0000 to 1001]. We have to use only two binary adders and give the output as the sum of given two 4 bit binary numbers in excess 3.

## Conclusion 5B

In this practical , We want the output of this excess 3 sum in 8 bit. So first we added two binary 4-bit numbers through adder. Then we divided the problem in two parts :

1. When carry is 0
2. When carry is 1

In First case, When Carry is 0 then the input binary number's sum is definitely from range 0 to 9. Then we simply have to subtract 3 from the sum, which can be done by using 1's complement method. Here we used another binary adder and it's result will give us addition of this two excess-3 numbers.

In Second case, When Carry is 1 then we have 8-bit output. Which can be obtained by : First 4 bits will sum and others four bits be 0100. This will give us the addition of this two excess -3 numbers. The first 4 bits showed the sum of output of first 4 bit adders with 3. And last 4 bits (i.e. leftmost 4 bits) showed 0100 value.

**Truth Table : Binary sum to BCD sum**

Decimal	Binary Sum					BCD Sum				
	C'	A'	B'	C'	D'	C	E	F	G	H
0	0	0	0	0	0	0	0	0	0	0
1	0	0	0	0	1	0	0	0	0	1
2	0	0	0	1	0	0	0	0	1	0
3	0	0	0	1	1	0	0	0	1	1
4	0	0	1	0	0	0	0	1	0	0
5	0	0	1	0	1	0	0	1	0	1
6	0	0	1	1	0	0	0	1	1	0
7	0	0	1	1	1	0	0	1	1	1
8	0	1	0	0	0	0	1	0	0	0
9	0	1	0	0	1	0	1	0	0	1
10	0	1	0	1	0	1	0	0	0	0
11	0	1	0	1	1	1	0	0	0	1
12	0	1	1	0	0	1	0	0	1	0
13	0	1	1	0	1	1	0	0	1	1
14	0	1	1	1	0	1	0	1	0	0
15	0	1	1	1	1	1	0	1	0	1
16	1	0	0	0	0	1	0	1	1	0
17	1	0	0	0	1	1	0	1	1	1
18	1	0	0	1	0	1	1	0	0	0
19	1	0	0	1	1	1	1	0	0	1

### Truth Table : Excess 3 parallel adder

Original (A+B)	Excess 3 of A + Excess 3 of B	Excess 6 of (A+B)					Excess 3 of(A+B)							
		E	A	B	C	D	E	F	G	H	A	B	C	D
0	6	0	0	1	1	0	0	0	0	0	0	0	1	1
1	7	0	0	1	1	1	0	0	0	0	0	1	0	0
2	8	0	1	0	0	0	0	0	0	0	0	1	0	1
3	9	0	1	0	0	1	0	0	0	0	0	1	1	0
4	10	0	1	0	1	0	0	0	0	0	0	1	1	1
5	11	0	1	0	1	1	0	0	0	0	1	0	0	0
6	12	0	1	1	0	0	0	0	0	0	1	0	0	1
7	13	0	1	1	0	1	0	0	0	0	1	0	1	0
8	14	0	1	1	1	0	0	0	0	0	1	0	1	1
9	15	0	1	1	1	1	0	0	0	0	1	1	0	0
10	16	1	0	0	0	0	0	1	0	0	0	0	1	1
11	17	1	0	0	0	1	0	1	0	0	0	1	0	0
12	18	1	0	0	1	0	0	1	0	0	0	1	0	1
13	19	1	0	0	1	1	0	1	0	0	0	1	1	0
14	20	1	0	1	0	0	0	1	0	0	0	1	1	1